

VHDL

5051158-xxxx

Lecture 3

Digital logic basics - sequential logic


VHDL Basics – part 2

Contents of this lecture

- Digital logic basics (sequential logic)
- VHDL basics
 - for creating sequential logic
 - VHDL “program structure”

Digital logic basics – sequential logic

Synchronous logic – flip flops

 





- Most commonly used: D-flip-flop
- D is sampled on a rising edge of CLK signal:
 - D is copied to Q
 - An inverted output, Q' is provided as well
- The output state is maintained until the next rising edge of the clock
- In essence, this is a single bit memory
- Can have (and usually has) other ports:
 - Reset/Clear (RST, CLR), often active low): Forces Q to '0' (and Q' to '1')
 - Set (S): Forces Q to '1' (and Q' to '0')
 - Enable (ENA): If '0', clock is “masked”, clock edge has no effect

```
entity DFF_rstLow is
    port(
        Q : out std_logic;
        Clk,n_Rst,D :in std_logic);
end DFF_rstLow;

architecture rtl of DFF_rstLow is
begin
    process (Clk,n_Rst)
    begin
        if(n_Rst='0') then
            Q <= '0';
        elsif(rising_edge(Clk)) then
            Q <= D;
        end if;
    end process;
end rtl;
```


Synchronous logic – (async) counters (1)

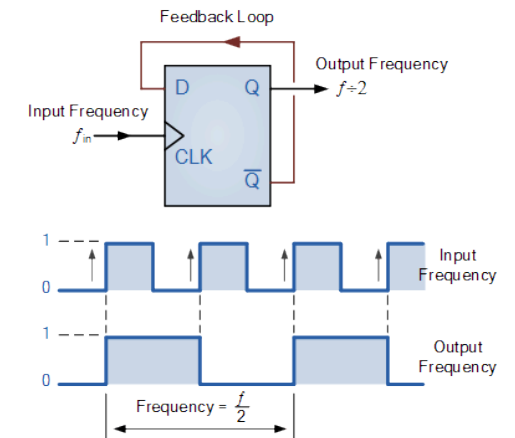 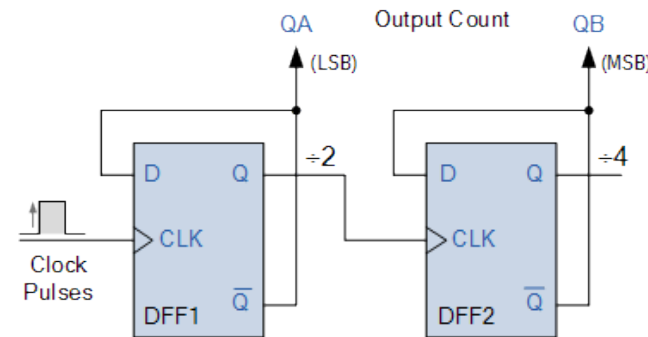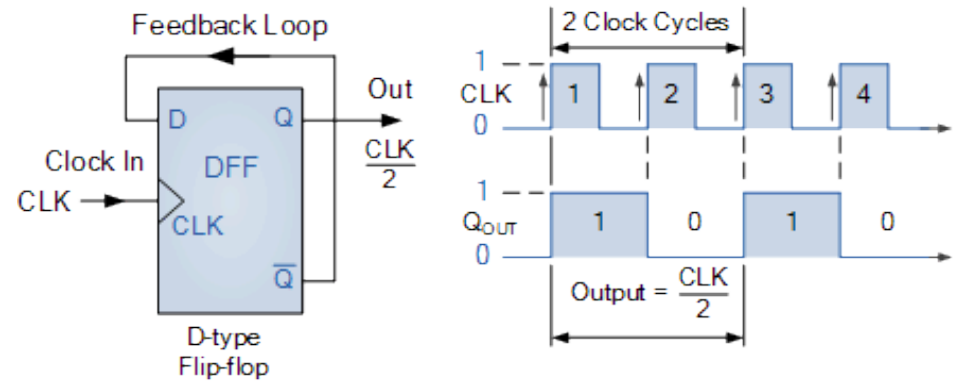- A D-flipflop can be used as a clock divider: Route Q' to D and apply CLK to clock input: Q changes state every other clock cycle
 - Divide-by-Two-Counter (modulo 2 counter)
- By cascading these, i.e. connecting Q' to CLK of the next register, we have a ripple counter (Mod-4-counter)






Synchronous logic – (async) counters (2)

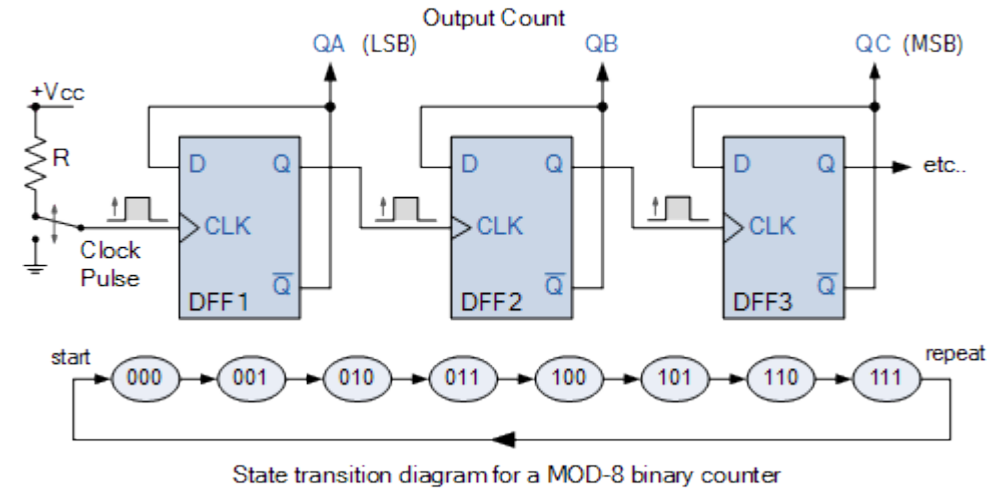- In a similar way, we can create longer counters
- Long ripple counters have one fundamental problem: After a clock edge, it takes some time until all the bits are changed -> This limits the maximum clock speed



Modulo-N (async) counters

 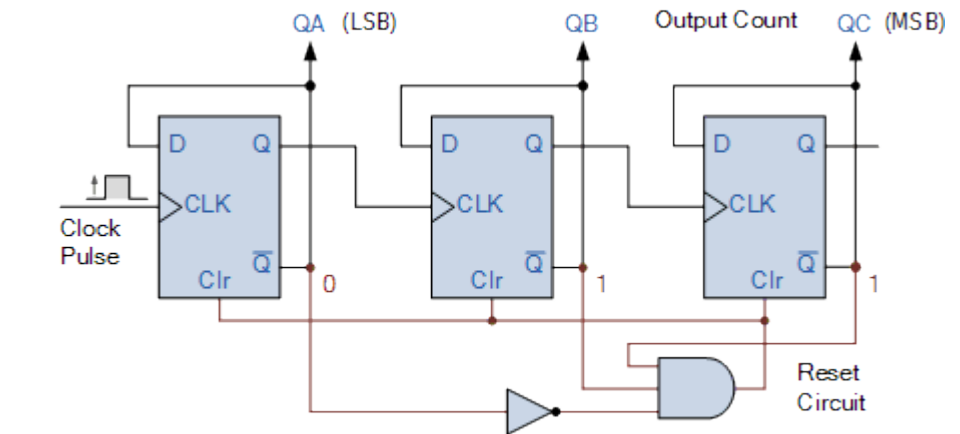
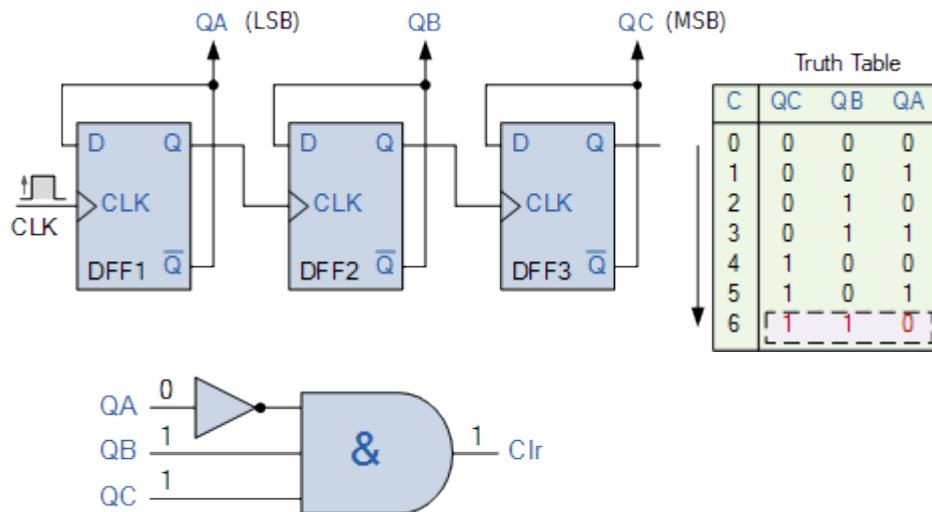
- Modulo N-counter, where $N = 2^x$ are easy: the counter wraps over. If not, a reset condition is required
- Example: Mod-5 - counter



Synchronous counters


- To overcome the timing problem with asynchronous ripple-counters, we need to use synchronous counters instead
- This can be achieved (for example) by using T-flip-flops instead
 - The output toggles (changes state) on clock edge IF the input T is '1' – otherwise no change
- D-flip-flops can be converted to T-flip-flop
- By cascading these, we'll get a synchronous (BCD) counter

Q_n	T	$Q_n + 1$
0	0	0
0	1	1
1	0	1
1	1	0

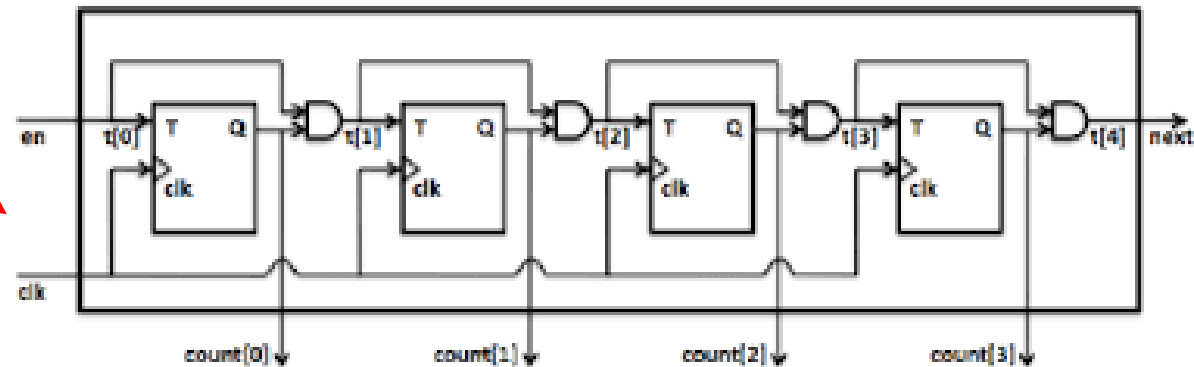 

Counters in VHDL – Modulo 16

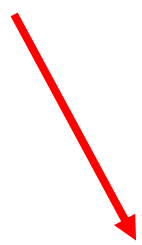These libraries define how to handle arithmetic operations with std_logic



```
library IEEE;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

use IEEE.STD_LOGIC_1164.ALL;

entity Counter16 is
    port( Clk, Ena, n_Rst: in std_logic;
          Q: out std_logic_vector(3 downto 0));
end Counter16;
```

```
architecture rtl of Counter16 is
    signal Cnt_int: std_logic_vector(3 downto 0);
begin
    process(Clk,n_Rst)
    begin
        if n_Rst='0' then
            Cnt_int <= (others => '0');
        elsif(rising_edge(Clk)) then
            if Ena='1' then
                Cnt_int <= Cnt_int + 1;
            end if;
        end if;
    end process;
    Q <= Cnt_int;
end rtl;
```

Counters in VHDL – Modulo 10

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity Counter16 is
    port( Clk, Ena, n_Rst: in std_logic;
          Q: out std_logic_vector(3 downto 0));
end Counter16;
```

Reset (wrap around)
condition defined here



```
architecture rtl of Counter16 is
    signal Cnt_int: std_logic_vector(3 downto 0);
begin
    process(Clk, n_Rst)
    begin
        if n_Rst='0' then
            Cnt_int <= (others => '0');
        elsif(rising_edge(Clk)) then
            if Ena='1' then
                if Cnt_int="1001" then
                    Cnt_int <= (others => '0');
                else
                    Cnt_int <= Cnt_int + 1;
                end if;
            end if;
        end if;
    end process;
    Q <= Cnt_int;
end rtl;
```

VHDL “program” structure

VHDL “program” structure

- Libraries

- Adds extra packages, like *#include*-statements in C, or *import* in Python

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;
```

- Entity

- Generics
- Ports

```
entity led_thingy_top_2 is  
    Port ( btn : in STD_LOGIC_VECTOR (3 downto 0);  
          led4_r : out std_logic;  
          led4_g : out std_logic;  
          led4_b : out std_logic;  
    );  
end led_thingy_top_2;
```

- Architecture

- Component declarations
- Signal declarations
- Component instantiations
- Concurrent statements
- Processes

```
architecture rtl of led_thingy_top_2 is
```

```
-- RGB driver  
component RGB_Driver  
    Port (  
        Buttons : in std_logic_vector (1 downto 0);  
        RGB_out : out std_logic_vector (0 to 2));  
end component;
```

```
-- group of RGB led signals  
signal RGB_Led_4: std_logic_vector(0 to 2);
```

```
begin
```

VHDL “program” structure (cont)

- Architecture

- ...
- Component instantiations
- Concurrent statements
- Processes (not shown here)

```
architecture rtl of led_thingy_top_2 is
```

```
...
```

```
begin
```

```
-- component instantiations
```

```
i_RGB4_Driver: RGB_Driver
```

```
port map (
```

```
    Buttons => btn(1 downto 0),
```

```
    RGB_Out => RGB_Led_4
```

```
);
```

```
-- map signal "RGB_Led_4" to actual output ports
```

```
led4_r <= RGB_Led_4(2);
```

```
led4_g <= RGB_Led_4(1);
```

```
led4_b <= RGB_Led_4(0);
```

```
end rtl;
```

VHDL Components and hierarchical design

- A component declaration declares a virtual design entity interface that may be used in component **instantiation** statement
- A component represents an entity/architecture pair. It specifies a subsystem, which can be **instantiated in another architecture** leading to a hierarchical specification.
 - Component instantiation is like plugging a hardware component into a socket in a board
- A component must be **declared** before it is **instantiated**
 - The component declaration defines the virtual interface of the instantiated design entity ("the socket")
- Most often, the declaration takes in the main code (in the architecture, before "begin") or in separate packages (more on this later)
- Generics and ports of a component are **copies** of generics and ports of the entity the component represents.

```
component component_name is
    generic (generic_list);
    port (port_list);
end
component component_name;
```

```
architecture rtl of xxx is
```

```
    component XOR_4 is
        port(A,B: in std_logic_vector(0 to 3);
              C: out std_logic_vector(0 to 3));
    end component XOR_4;
```

```
    signal S1,S2 : std_logic_vector(0 to 3);
    signal S3 : std_logic_vector(0 to 3);
```

```
begin
```

```
    X1 : XOR_4
    port map(A => S1,B => S2,C => S3);
```

```
end architecture rtl;
```