

VHDL

5051158-xxxx

Lecture 2

Digital logic basics - combinatorial logic

VHDL Basics – part 1


Contents of this lecture

- Digital logic basics (combinatorial logic)
- VHDL basics (for creating combinatorial logic)

Digital logic basics – combinatorial logic


Logic gates

NOT

 


Inputs		Output
A	B	
0	1	
1	0	

AND

 


Inputs		Output
A	B	AB
0	0	0
0	1	0
1	0	0
1	1	1

OR

 

Inputs		Output
A	B	A + B
0	0	0
0	1	1
1	0	1
1	1	1

XOR

 

Inputs		Output
A	B	A ⊕ B
0	0	0
0	1	1
1	0	1
1	1	0

- Basic building blocks for all the digital logic
- The examples are 2-input gates, but there are wider gates as well (like 4-input ANDs and so on)

VHDL: `Y <= not A;`

`Y <= A and B;`


`Y <= A or B;`

`Y <= A xor B;`

https://www.tutorialspoint.com/computer_logical_organization/logic_gates.htm


Logic gates (inverted output)

NAND

 


Inputs		Output
A	B	\overline{AB}
0	0	1
0	1	1
1	0	1
1	1	0

NOR

 

Inputs		Output
A	B	$\overline{A+B}$
0	0	1
0	1	0
1	0	0
1	1	0

XNOR

 

Inputs		Output
A	B	$A \oplus B$
0	0	1
0	1	0
1	0	0
1	1	1

- NAND is all you need:
 - A NAND B, where $A=B$ is an inverter (NOT)
 - NAND becomes OR (and vice versa) if all the inputs and output are inverted (DeMorgan's theorems)

VHDL: `Y <= A nand B;`


`Y <= A nor B;`

`Y <= A xnor B;`

https://www.tutorialspoint.com/computer_logical_organization/demorgan_theroems.htm


The drawing symbols vary...

- US style clearly the most popular

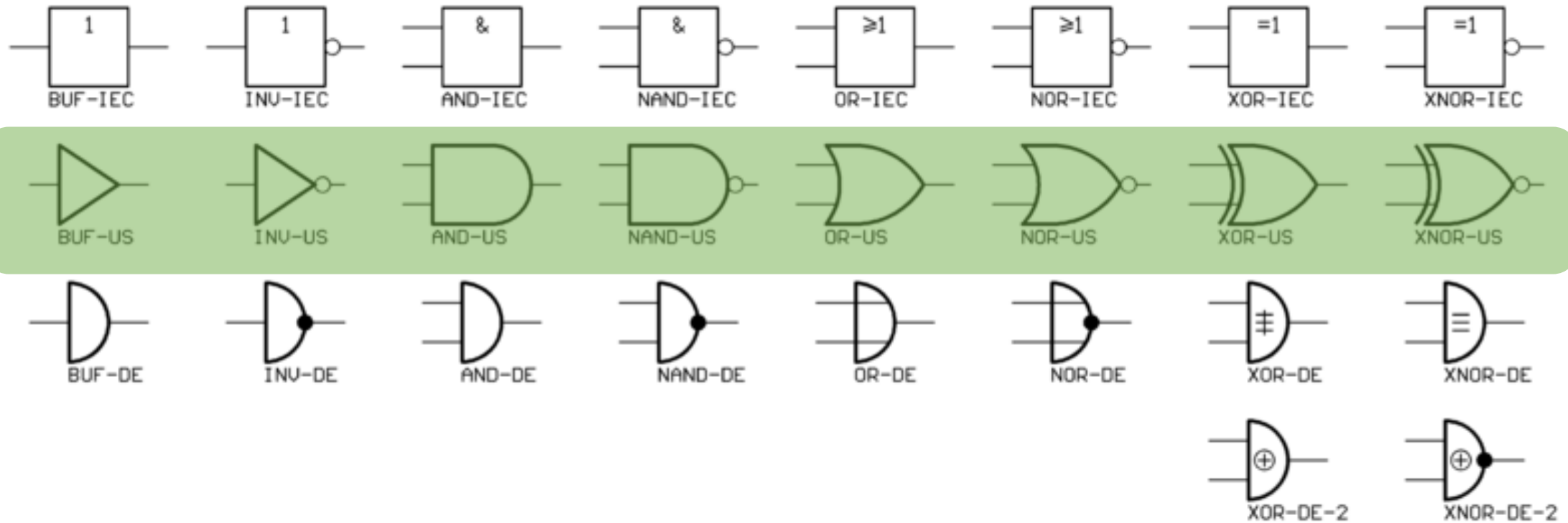


Why NAND/NOR-gates are favored in actual implementations?

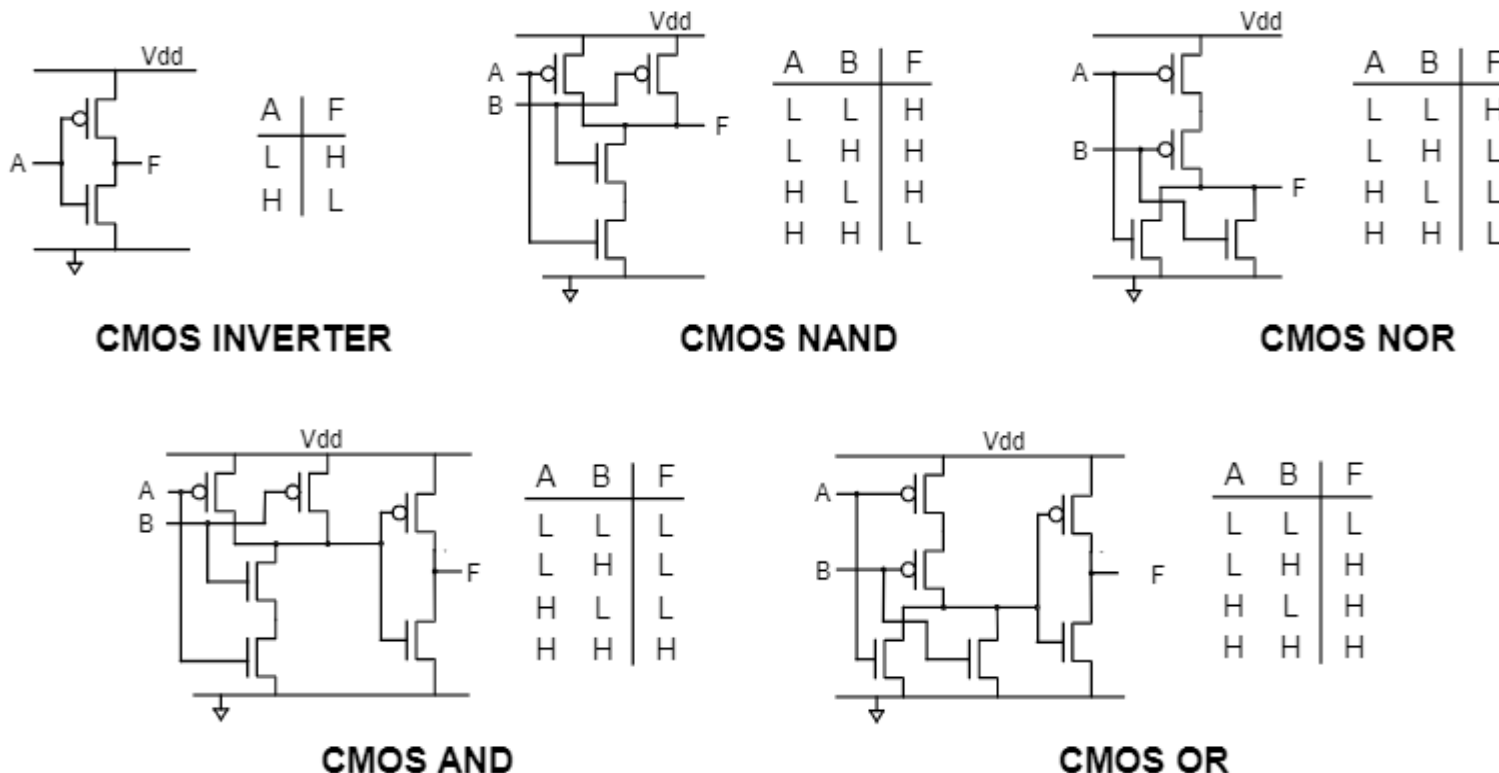- Because they require 2 (CMOS) transistors less than AND/OR
- Less transistors = smaller, cheaper, less power, faster (at least in this case)



What is combinatorial logic?



- Unlike Sequential Logic Circuits whose outputs are dependant on both their present inputs and their previous output state giving them some form of *Memory*. The outputs of **Combinational Logic Circuits** are only determined by the logical function of their current input state, logic “0” or logic “1”, at any given instant in time.
- The result is that combinational logic circuits have no feedback, and any changes to the signals being applied to their inputs will immediately* have an effect at the output. In other words, in a **Combinational Logic Circuit**, the output is dependant at all times on the combination of its inputs. Thus a combinational circuit is *memoryless*.

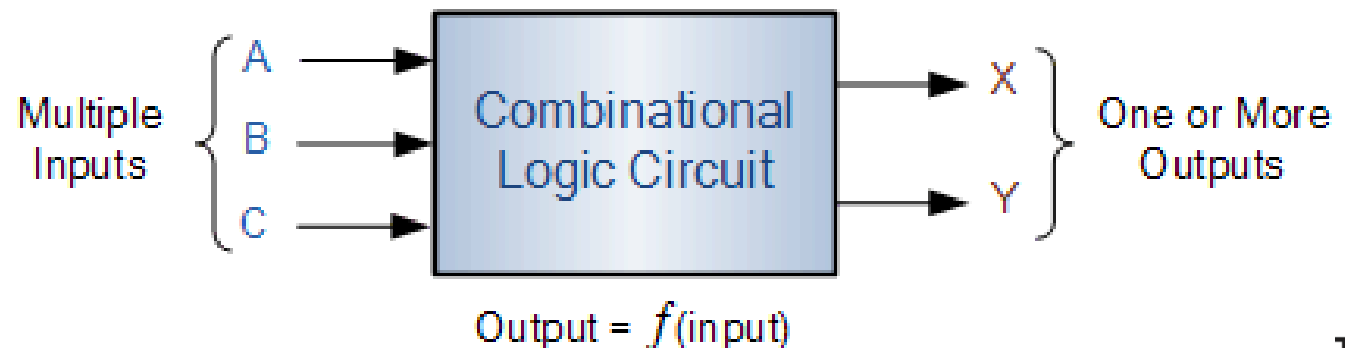

* actually, there is propagation delay always

Combinatorial logic circuits – Multiplexer (MUX)

  - Selects “one input out of many” to single output
- Example: 4-to-1 mux



B	A	Y
0	0	D0
0	1	D1
1	0	D2
1	1	D3

Note: Inputs D0-D3 are not just static '0's or '1's – they can be any logic signals or signal buses carrying data, clocks, even at different frequencies

```
s <= (B, A); -- just a helper
with s select
  Y <= D0 when "00",
        D1 when "01",
        D2 when "10",
        D3 when others;
```

MUX in VHDL (in architecture)

- Conditional Signal Assignment

```
Y <= A when (s = "00") else  
    B when (s = "01") else  
    C when (s = "10") else  
    D;
```

- Selective Signal Assignment

```
with s select  
    Y <= D0 when "00",  
        D1 when "01",  
        D2 when "10",  
        D3 when others;
```

MUX in VHDL (inside processes)

- Using if-elsif-else -statements



```
process (A,B,C,D,s) is
begin
    if (s = "00") then
        Y <= A;
    elsif (s = "01") then
        Y <= B;
    elsif (s = "10") then
        Y <= C;
    else
        Y <= D;
    end if;
end process;
```

- Using case-statement

```
mux : process (A,B,C,D,s) is
begin
    case s is
        when "00" => Y <= A;
        when "01" => Y <= B;
        when "10" => Y <= C;
        when others => Y <= D;
    end case;
end process mux;
```

Comb. logic circuits – Demultiplexer (DEMUX)

  - Maps “one input to one of many outputs”
- Example: 1-to-4 demux



B	A	D0	D1	D2	D3
0	0	X	0	0	0
0	1	0	X	0	0
1	0	0	0	X	0
1	1	0	0	0	X

Assuming $X = '1'$, this becomes 2-to-4 “one-hot” decoder
Of course, ‘X’ can be a data stream or a clock signal, so demux is “routing” the signal.